


姓名：

(號)

成績

年級：

科目：

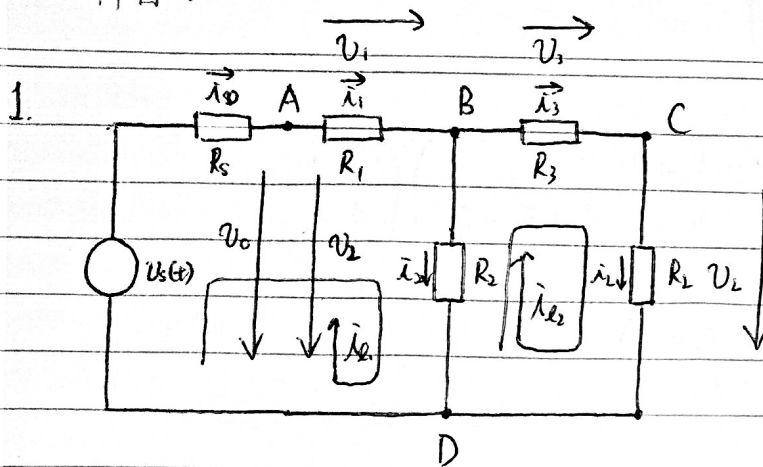

支路電壓電流法

$$\left. \begin{aligned} i_0 R_s + V_0 &= V_s \\ i_1 R_1 - V_1 &= 0 \\ i_2 R_2 - V_2 &= 0 \\ i_3 R_3 - V_3 &= 0 \\ i_L R_L - V_L &= 0 \end{aligned} \right\} \text{五條支路}$$

$$\left. \begin{aligned} i_0 - i_1 &= 0 \\ i_1 - i_2 - i_3 &= 0 \\ i_3 - i_L &= 0 \end{aligned} \right\} \text{結點電流 KCL 方程}$$

$$\begin{aligned} i_1 R_1 + i_2 R_2 - V_0 &= 0 \\ \bar{x} \end{aligned}$$

$$\left. \begin{aligned} V_1 + V_2 - V_0 &= 0 \\ V_3 + V_L - V_2 &= 0 \end{aligned} \right\} \text{回路電壓 KVL 方程}$$

支路電流法

(同上的三條 KCL 方程)

$$\left. \begin{aligned} i_0 R_s + i_1 R_1 + i_2 R_2 &= V_s \\ i_3 R_3 + i_L R_L - i_2 R_2 &= 0 \end{aligned} \right\} \text{回路電壓 KVL 方程}$$

回路電流法

$$\left. \begin{aligned} i_{L1} &= i_1 \quad \text{因} \quad i_{L1} (R_s + R_1 + R_2) - i_{L2} R_2 = V_s \\ i_{L2} &= i_3 \quad i_{L2} (R_3 + R_L + R_2) - i_{L1} R_2 = 0 \end{aligned} \right\} \text{KVL 方程}$$

結點電壓法 (不妨設 $V_D = 0V$)

$$\frac{V_s - V_A}{R_s} = \frac{V_A - V_B}{R_1}$$

$$\frac{V_A - V_B}{R_1} = \frac{V_B - V_C}{R_3} + \frac{V_B - V_D}{R_2}$$

$$\frac{V_B - V_C}{R_3} = \frac{V_C - V_D}{R_L}$$

KCL 方程

利用回路電流法對方程求解

$$\begin{pmatrix} R_3 + R_1 + R_2 & -R_2 \\ -R_2 & R_3 + R_L + R_2 \end{pmatrix} \begin{pmatrix} \dot{\lambda}_1 \\ \dot{\lambda}_2 \end{pmatrix} = \begin{pmatrix} V_S \\ 0 \end{pmatrix}$$


$$\begin{pmatrix} \dot{\lambda}_1 \\ \dot{\lambda}_2 \end{pmatrix} = \frac{1}{(R_3 + R_1 + R_2)(R_3 + R_L + R_2) - R_2^2} \begin{pmatrix} R_3 + R_L + R_2 & R_2 \\ R_2 & R_3 + R_1 + R_2 \end{pmatrix} \begin{pmatrix} V_S \\ 0 \end{pmatrix}$$

$$= \frac{V_S}{(R_3 + R_1 + R_2)(R_3 + R_L + R_2) - R_2^2} \begin{pmatrix} R_3 + R_L + R_2 \\ R_2 \end{pmatrix}$$

$$V_L = \dot{\lambda}_2 R_L = \dot{\lambda}_2 R_L = \frac{R_2 R_L}{(R_3 + R_1 + R_2)(R_3 + R_L + R_2) - R_2^2} V_S$$

$$\text{衰減係數} = \frac{P_{S, \max}}{P_{L, \text{rms}}} = \frac{\frac{1}{4R_S} \overline{V_S^2}}{\frac{1}{R_L} \overline{V_L^2}} = \frac{R_L}{4R_S} \left(\frac{(R_3 + R_1 + R_2)(R_3 + R_L + R_2) - R_2^2}{R_2 R_L} \right)^2$$
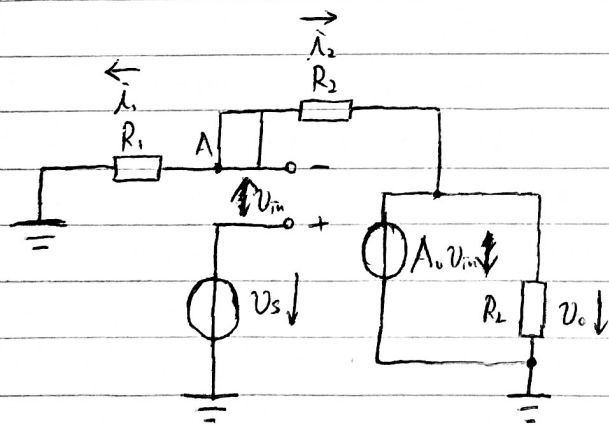
$$= \frac{1}{4} \left(\frac{111^2 - 35^2}{35 \times 50} \right)^2 = 10.05$$



分析A結果

$$\dot{\lambda}_1 = \dot{\lambda}_2 \quad \dot{\lambda}_1 + \dot{\lambda}_2 = 0$$


$$\Leftrightarrow \frac{V_S - V_{in}}{R_1} + \frac{V_S - V_{in} - A_0 V_{in}}{R_L} = 0$$

$$\Leftrightarrow V_{in} = \frac{V_S (G_1 + G_2)}{G_1 + (A_0 + 1)G_2}$$

$$\Rightarrow V_o = A_0 V_{in} = \frac{A_0 (G_1 + G_2)}{G_1 + (A_0 + 1)G_2} V_S = \frac{A_0 (1 + \frac{R_1}{R_2})}{1 + (A_0 + 1)\frac{R_1}{R_2}} V_S$$

$$\lim_{A \rightarrow \infty} \frac{V_o}{V_S} = \frac{1 + \frac{R_1}{R_2}}{\frac{R_1}{R_2}} = 1 + \frac{R_2}{R_1}, \text{ 即當 } A \text{ 充分大時, 放大倍數只與電阻比有關}$$

3.

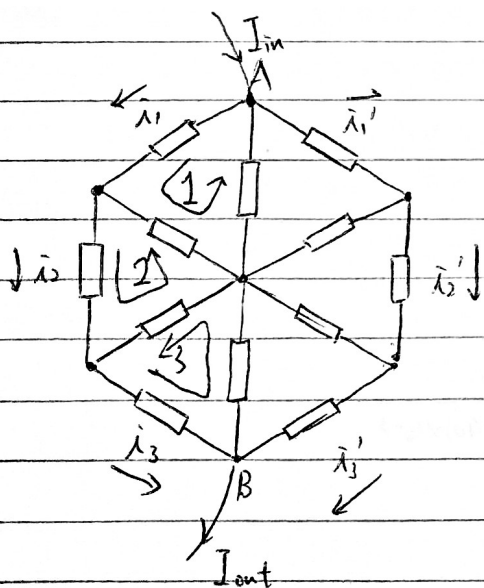

不妨假设在A,B端施加电压 $U = U_A - U_B (>0)$

由对称性知 $\lambda_1 = \lambda_1'$, $\lambda_2 = \lambda_2'$, $\lambda_3 = \lambda_3'$ 。又知 $I_{in} = I_{out}$

$$\lambda_1 R + (\lambda_1 - \lambda_2) R + (\lambda_1 + \lambda_1' - I_{in}) R = 0$$

$$\text{回路 1. } 4\lambda_1 - \lambda_2 = I_{in}$$

$$\lambda_2 R + (\lambda_2 - \lambda_3) R + (\lambda_2 - \lambda_1) R = 0$$

$$\text{回路 2. } \lambda_1 - 3\lambda_2 + \lambda_3 = 0$$

$$\lambda_3 R + (\lambda_3 + \lambda_3 - I_{out}) R + (\lambda_3 - \lambda_2) R = 0$$

$$\text{回路 3. } \lambda_2 - 4\lambda_3 = -I_{out} = -I_{in}$$


$$\text{联立回路 1 和回路 2, } \lambda_1 - 3(4\lambda_1 - I_{in}) + \lambda_3 = 0 \Leftrightarrow 11\lambda_1 - \lambda_3 = 3I_{in}$$

$$\text{联立回路 1 和回路 3, } 4(\lambda_1 - \lambda_3) = 0 \Leftrightarrow \lambda_1 = \lambda_3$$

$$\Rightarrow \begin{pmatrix} \lambda_1 \\ \lambda_2 \\ \lambda_3 \end{pmatrix} = \begin{pmatrix} 0.3 \\ 0.2 \\ 0.3 \end{pmatrix} I_{in}, \quad I_{in} R_{AB} = U = \lambda_1 R + \lambda_2 R + \lambda_3 R = 0.8 I_{in} R$$

$$\Rightarrow R_{AB} = 0.8R = 0.8\Omega$$

4. 原电路等效化简

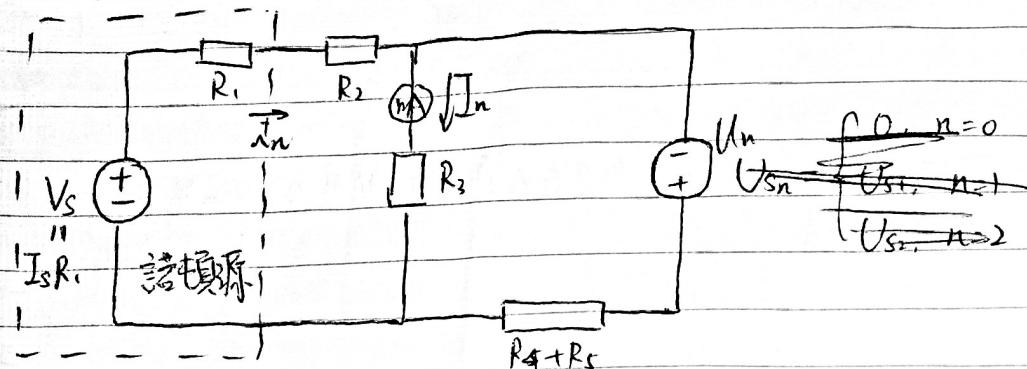

其中 $U_n = \begin{cases} 0, & n=1 \\ U_{s1} = 10V, & n=2 \\ U_{s3} = 15V, & n=3 \end{cases}$

$$\begin{cases} V_s = i_n (R_1 + R_2) + I_n R_3 \\ U_n = (i_n - I_n) (R_4 + R_5) - I_n R_3 \end{cases} \Leftrightarrow \begin{cases} V_s - I_n R_3 = i_n (R_1 + R_2) \\ U_n + I_n (R_3 + R_4 + R_5) = i_n (R_4 + R_5) \end{cases}$$

$$\Leftrightarrow (V_s - I_n R_3) (R_4 + R_5) = (U_n + I_n (R_3 + R_4 + R_5)) (R_1 + R_2)$$

$$\Leftrightarrow V_s (R_4 + R_5) = (U_n + I_n (R_3 + R_4 + R_5)) (R_1 + R_2) + I_n R_3 (R_4 + R_5)$$

$$\Leftrightarrow \frac{V_s (R_4 + R_5)}{R_1 + R_2} = U_n + I_n \left(R_3 + R_4 + R_5 + \frac{R_3 (R_4 + R_5)}{R_1 + R_2} \right)$$

$$\Rightarrow \text{记 } R = R_3 + R_4 + R_5 + \frac{R_3 (R_4 + R_5)}{R_1 + R_2}, \quad U = \frac{V_s (R_4 + R_5)}{R_1 + R_2}$$

$$\text{则 } U_{n+1} - U_n + (I_{n+1} - I_n) R = 0$$

$$\Leftrightarrow R = \frac{U_n - U_{n+1}}{I_{n+1} - I_n} = \frac{U_1 - U_2}{I_2 - I_1} = \frac{0 - 10}{(-60 - 40) \times 10^{-3}} = 100 \Omega$$

$$\Rightarrow U = I_1 R = 4V$$

$$\text{因此 } 4V = 15V + I_3 \times 100 \Omega \Leftrightarrow I_3 = -110 \text{ mA}$$