



清華大學

1. (1) 當 $R=10k\Omega$ 時, $V_D = V_{DD} - I_D R = 2.5V - 50\mu A \times 10k\Omega = 2V$

$\Rightarrow V_{GD} = V_{in} - V_D = 0V < V_T$, M_1 工作在飽和區

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{GT} - V_S)^2$$

$$\Rightarrow V_S = V_{in} - V_T - \sqrt{\frac{2I_D}{k_n' \left(\frac{W}{L} \right)}} = 1.30V$$

(2) 當 $R=30k\Omega$ 時, $V_D = V_{DD} - I_D R = 2.5V - 50\mu A \times 30k\Omega = 1V$

$\Rightarrow V_{GD} = V_{in} - V_D = 2V - 1V = 1V > V_T$, M_1 不工作在飽和區

若 M_1 工作區在速度飽和區, 則有 $V_{GS} > V_T$ 且 $V_{DS} > V_{DSAT}$

$$\Leftrightarrow V_S < \min(V_{in} - V_T, V_D - V_{DSAT}) = 0.4V$$

顯然 $V_S = 0.4V$ 便是 M_1 的線性區和速度飽和區的分界

$$\text{此時 } I_D = k_n' \left(\frac{W}{L} \right) V_{DSAT} (V_{in} - V_S - V_T - 0.5V_{DSAT}) = 594\mu A \neq I_D, \text{ 矛盾}$$

所以 M_1 工作在線性區

$$I_D = k_n' \left(\frac{W}{L} \right) (V_D - V_S) [V_{in} - V_S - V_T - 0.5(V_D - V_S)]$$

$$50 = 1100 (1 - V_S) (1.1 - 0.5V_S)$$

$$5 = 55V_S^2 - 176V_S + 121 \Leftrightarrow 55V_S^2 - 176V_S + 116 = 0$$

$$V_S = \frac{176 \pm \sqrt{176^2 - 4 \times 55 \times 116}}{110} = \frac{88 \pm \sqrt{88^2 - 55 \times 116}}{55} = \frac{88 - \sqrt{88^2 - 55 \times 116}}{55} = 0.93V$$

(3) 當 $R=10k\Omega$ 且 $\lambda \neq 0$ 時,

$$I_D = \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{in} - V_T - V_S) [1 + \lambda(V_D - V_S)]$$

若 V_S 下降, 則 I_D 上升, 比 I_D 大, 矛盾.

所以 V_S 只能升高

2. (i) : 若 M₁ 工作在饱和区, 则 $V_i - V_o > V_T(V_o) = V_{T0} + \gamma(\sqrt{1-2\phi_F + V_{o1}} - \sqrt{1-2\phi_F})$
 $= V_{T0} + \gamma(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|})$
 $V_i - V_{DD} < V_T(V_o) \Rightarrow$

~~$\Rightarrow V_o + V_{T0} + \gamma(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|})$~~

~~$\Rightarrow V_{DD} + V_o < V_{T0} + V_o + \gamma(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|})$~~

$\Rightarrow V_o + V_T(V_o) < V_i < V_{DD} + V_T(V_o)$

$I_o = \frac{1}{2}k_n' \left(\frac{W}{L}\right) (V_i - V_o - V_T(V_o))^2 \dots (1)$

设 $V_{Def} = V_{T0} - \gamma\sqrt{2|\phi_F|} + \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)}$

ii. 若 M₁ 工作在线性区, 则 ~~$V_i > V_o + V_T(V_o)$~~ $V_i > \max(V_o, V_{DD}) + V_T(V_o)$

$I_o = k_n' \left(\frac{W}{L}\right) (V_{DD} - V_o) [V_{in} - V_o - V_T(V_o) - 0.5(V_{DD} - V_o)] \dots (2)$

(1) 式: $I_o = \frac{1}{2}k_n' \left(\frac{W}{L}\right) [V_i - V_o - V_{T0} - \gamma(\sqrt{1-2\phi_F + V_{o1}} - \sqrt{2|\phi_F|})]^2$

$\Leftrightarrow V_o + \gamma\sqrt{1-2\phi_F + V_o} = V_i - V_{T0} + \gamma\sqrt{2|\phi_F|} + \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)} = V_i - V_{Def}$

$\Leftrightarrow \gamma^2(1-2\phi_F + V_o) = (V_i - V_{Def})^2 - 2(V_i - V_{Def})V_{T0} + V_{T0}^2$

$\gamma^4(V_o - 2\phi_F)^2 = [V_o - (V_i - V_{Def})]^4 \quad \boxed{V_i = V_o + \gamma\sqrt{1-2\phi_F + V_o} + V_{Def}} \quad (1^*)$

$\Leftrightarrow [V_o^2 - (2V_i - 2V_{Def} + \gamma^2)V_o + (V_i - V_{Def})^2 + 2\gamma^2\phi_F][V_o^2 - (2V_i - 2V_{Def} - \gamma^2)V_o + (V_i - V_{Def})^2 - 2\gamma^2\phi_F] =$

$V_o = \frac{2V_i - 2V_{Def} + \gamma^2 \pm \sqrt{(2V_i - 2V_{Def} + \gamma^2)^2 - 4[(V_i - V_{Def})^2 + 2\gamma^2\phi_F]}}{2} \quad \text{或} \quad \frac{2V_i - 2V_{Def} - \gamma^2 \pm \sqrt{(2V_i - 2V_{Def} - \gamma^2)^2 - 4[(V_i - V_{Def})^2 - 2\gamma^2\phi_F]}}{2}$

$= \frac{2V_i - 2V_{Def} + \gamma^2 \pm \sqrt{\gamma^2(4V_i - 4V_{Def} + \gamma^2) - 8\gamma^2\phi_F}}{2} \quad \text{或} \quad \frac{2V_i - 2V_{Def} - \gamma^2 \pm \sqrt{(\gamma^2 + 4V_{Def} - 4V_i)\gamma^2 + 8\gamma^2\phi_F}}{2}$

$= \frac{2V_i - 2V_{Def} + \gamma^2 \pm \gamma\sqrt{4V_i - 4V_{Def} + \gamma^2 - 8\phi_F}}{2} \quad \text{或} \quad \frac{2V_i - 2V_{Def} - \gamma^2 \pm \gamma\sqrt{8\phi_F - (4V_i - 4V_{Def} - \gamma^2)}}{2} \quad (\text{舍去})$

ii. 若 M₁ 工作在线性区

(2) 式: $I_o = k_n' \left(\frac{W}{L}\right) (V_{DD} - V_o) (V_{in} - V_o - V_{T0} - \gamma(\sqrt{1-2\phi_F + V_{o1}} - \sqrt{2|\phi_F|}) - 0.5V_{DD} + 0.5V_o)$

$V_i = \frac{\frac{I_o}{k_n'} \left(\frac{L}{W}\right)}{V_{DD} - V_o} + 0.5V_o + V_{T0} + 0.5V_{DD} + \gamma(\sqrt{1-2\phi_F + V_{o1}} - \sqrt{2|\phi_F|}) \quad (2^*)$

(1^{*}) 和 (2^{*}) 是 V_i 与 V_o 的函数关系。



清華大學

$$V_x = \begin{cases} V_o + \gamma \sqrt{1-2\phi_F + V_o} + V_{T0} - \gamma \sqrt{2|\phi_F|} + \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)}, & V_o < V_{DD} - \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)} = 2.13 \text{ V} \\ \frac{\frac{I_o}{k_n'} \left(\frac{L}{W}\right)}{V_{DD} - V_o} + 0.5(V_{DD} + V_o) + V_{T0} + \gamma \left(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|} \right), & V_o > 2.13 \text{ V} \end{cases}$$

$$V_T = V_{T0} + \gamma \left(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|} \right) = V_{T0} + \gamma \left(\sqrt{V_o - 2\phi_F} - \sqrt{-2\phi_F} \right)$$

$$\Rightarrow V_o = 2\phi_F + \left(\frac{V_T(V_o) - V_{T0}}{\gamma} + \sqrt{2|\phi_F|} \right)^2$$


$$\Rightarrow V_o = 2\phi_F + \left(\frac{V_T(V_o) - V_{T0}}{\gamma} + \sqrt{2|\phi_F|} \right)^2 + V_T(V_o) + \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)}, \quad V_o < 2.13 \text{ V}$$

$$V_x = \begin{cases} \frac{\frac{I_o}{k_n'} \left(\frac{L}{W}\right)}{V_{DD} - 2\phi_F - \left(\frac{V_T(V_o) - V_{T0}}{\gamma} + \sqrt{2|\phi_F|} \right)^2} + 0.5 \left(V_{DD} + 2\phi_F + \left(\frac{V_T(V_o) - V_{T0}}{\gamma} + \sqrt{2|\phi_F|} \right)^2 \right) + V_T(V_o), & V_o > 2.13 \text{ V} \end{cases}$$


若不考慮體效應，轉接額定值是 $V_{T0} + \sqrt{\frac{2I_o}{k_n'} \left(\frac{L}{W}\right)}$
 $= 0.80605 \text{ V}$

~~(2) $V_T = V_{T0} + \gamma \left(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|} \right)$ 考~~

$$(2) V_T = \begin{cases} V_{T0} + \gamma \left(\sqrt{1-2\phi_F + V_o} - \sqrt{2|\phi_F|} \right), & \text{考慮體效應} \\ V_{T0}, & \text{不考慮體效應} \end{cases}$$

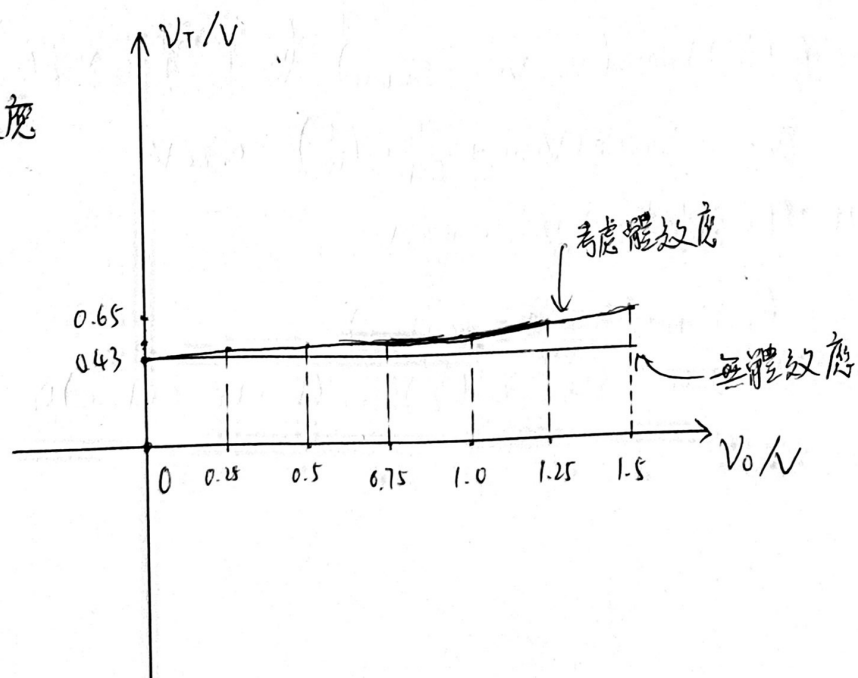

(3)

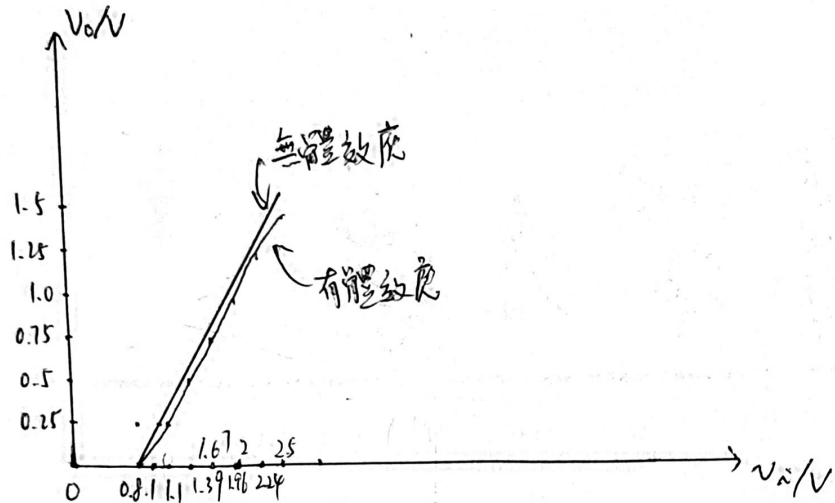

當 $V_o = 1.5V$ 時, 考慮體效應 $V_i = 2.5251V$

不考慮體效應 $V_i = 1.5V + 0.80605V = 2.30605V$

誤差 $0.21905V$



3. 当 $V_{in} < V_T = 0.4V$ 时, M_1 工作在截止区, $V_{out} = V_{DD} = 2.5V$

当 $V_{in} > 0.4V$ 时,

(i) 当 M_1 工作在饱和区, $V_{out} > V_{in} - V_T$

$$V_{out} = V_{DD} - I_D R_L = V_{DD} - \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{in} - V_T)^2 (1 + \lambda V_{out})$$

$$\Leftrightarrow V_{out} = \frac{V_{DD} + \frac{1}{\lambda}}{1 + \frac{1}{2} k_n' \left(\frac{W}{L} \right) (V_{in} - V_T)^2 \lambda R_L} - \frac{1}{\lambda} = \frac{8.05}{1 + 0.68 (V_{in} - 0.4)^2} - 6.25 (V)$$

(ii) 当 M_1 工作在速度饱和区, $V_{DSAT} < V_{out} < V_{in} - V_T$

$$V_{out} = V_{DD} - I_D R_L = V_{DD} - k_n' \left(\frac{W}{L} \right) V_{DSAT} (V_{in} - V_T - 0.5 V_{DSAT}) R_L (1 + \lambda V_{out})$$

$$= 2.5 - 3.825 (V_{in} - 0.625) = 2.5 - 3.825 (V_{in} - 0.625) (1 + \lambda V_{out})$$

$$V_{out} = \frac{V_{DD} + \frac{1}{\lambda}}{1 + k_n' \left(\frac{W}{L} \right) V_{DSAT} (V_{in} - V_T - 0.5 V_{DSAT}) \lambda R_L} - \frac{1}{\lambda} = \frac{8.05}{1 + 0.612 (V_{in} - 0.625)} - 6.25 (V)$$

(iii) 当 M_1 工作在线性区, $V_{out} < V_{DSAT}$

$$V_{out} = V_{DD} - k_n' \left(\frac{W}{L} \right) V_{out} (V_{in} - V_T - 0.5 V_{out}) (1 + \lambda V_{out}) R_L$$

饱和区与速度饱和区分界线: $0.68 (V_{in} - 0.4)^2 = 0.612 (V_{in} - 0.625)$

$$\cancel{0.68 V_{in}^2} \quad 10 V_{in}^2 - 8 V_{in} + 1.6 = \cancel{0.612} 9 V_{in} - 5.625$$

$$10 V_{in}^2 - 17 V_{in} + 7.225 = 0$$

$$100 V_{in}^2 - 170 V_{in} + 72.25 = 0$$

$$(10 V_{in} - 8.5)^2 = 0 \Leftrightarrow V_{in} = 0.85V$$

速度饱和区与线性区分界线

$$\frac{8.05}{1 + 0.612 (V_{in} - 0.625)} - 6.25 = 0.45$$

$$\frac{8.05}{6.70} - 1 = 0.612 (V_{in} - 0.625)$$

$$\Rightarrow V_{in} = \cancel{1.15} 0.95V$$

