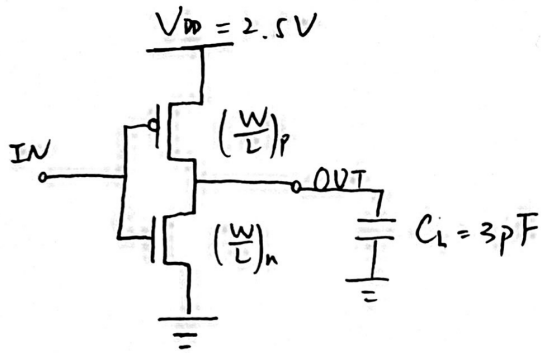


1.



	V_{TO}	γ	V_{DSAT}	k'	λ
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.01

$$I_{DSATP} = k'_p \left(\frac{W}{L} \right)_p \left((V_{GS} - V_{THP}) V_{DSAT} - 0.5 V_{DSAT}^2 \right)$$

$$t_{PLH} = \frac{C_L V_{DD}}{I_{DSATP}} = \frac{C_L V_{DD}}{I_{DSATP}}$$

$$\lambda = \frac{I_{DSATP} (1 + \lambda_p V_{DSAT})}{C_L} = \frac{C_L}{I_{DSATP} \lambda_p} \ln \left(\frac{1 - \frac{1}{2} \lambda_p V_{DD}}{1 - \lambda_p V_{DD}} \right)$$

$$0V \sim 1.25V : \lambda = -I_{DSATP} (1 + \lambda_p (V_{out} - V_{DD})) = C_L \frac{dV_{out}}{dt}$$

$$t_{PLH} = \frac{C_L}{\int_0^{V_{DD}} -I_{DSATP} \lambda_p} \ln \left(\frac{1 - \frac{1}{2} \lambda_p V_{DD}}{1 - \lambda_p V_{DD}} \right) = 2ns \Rightarrow \left(\frac{W}{L} \right)_p = 3.83 \times 10^1 \Leftrightarrow W_p = 7.58 \mu m$$

$$2.5V \sim 1.25V$$

$$I_{DSATN} (1 + \lambda_n V_{DSAT}) = -C_L \frac{dV_{out}}{dt}$$

$$t_{PHL} = \frac{C_L}{I_{DSATN} \lambda_n} \ln \left(\frac{1 + \lambda_n V_{DD}}{1 + \lambda_n \frac{V_{DD}}{2}} \right) = 2ns \Rightarrow \left(\frac{W}{L} \right)_n = 1.33 \times 10^1 \Leftrightarrow W_n = 3.31 \mu m$$

$$I_{DSAT} = k' \left(\frac{W}{L} \right) \left((V_{GS} - V_{TH}) V_{DSAT} - 0.5 V_{DSAT}^2 \right)$$

$$(V_{GS} = 0V) \quad I_{DSATP} = -30 \times 10^{-6} \times \left(\frac{W}{L} \right)_p \times (-1) \times (-2.5 + 0.4 - 0.5 \times (-1))$$

$$= -4.8 \times 10^{-5} \left(\frac{W}{L} \right)_p \text{ (A)}$$

$$(V_{GS} = 2.5V) \quad I_{DSATN} = 115 \times 10^{-6} \times \left(\frac{W}{L} \right)_n \times 0.63 \times (2.5 - 0.43 - 0.5 \times 0.63)$$

$$= 1.27 \times 10^{-4} \left(\frac{W}{L} \right)_n \text{ (A)}$$

Spice 仿真: $t_{pHL} = 2.218ns$, $t_{pLH} = 1.829ns$

$$2. \quad f = \sqrt[3]{F} = \sqrt[3]{\frac{C_L}{C_{in,1}}} = 6.69$$

$$t_p = 3t_{p0} (1 + \frac{\sqrt[3]{F}}{f}) = 3 \times 0.03 \times (1 + 6.69) = 0.692ns$$

第一级: $W_p = 1.2\mu m$, $W_n = 0.5\mu m$

第二级: $W_p = 8.03\mu m$, $W_n = 3.345\mu m$

第三级: $W_p = 53.7\mu m$, $W_n = 22.38\mu m$

Spice 仿真: $t_{pHL} = 689.7ps$, $t_{pLH} = 703.1ps$

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} = 696.10ps$$

$$3. \quad N=4, \quad h = \sqrt[4]{H} = \sqrt[4]{\frac{C_L}{C_{in}}} = \sqrt[4]{25}$$

$$N=4, \quad F = \frac{C_L}{C_{in}} = \frac{50 C_{ref}}{2 C_{ref}} = 25, \quad b_1 = \frac{C_{in} + C_{out} + 10 C_{ref}}{C_{in}} = b_2 = b_3 = b_4 = 1$$

$$g_1 = g_4 = 1, \quad g_2 = \frac{5}{3}, \quad g_3 = \frac{3+2}{1+2} = \frac{5}{3}$$

$$G = \frac{25}{9}$$

$$3. \quad N=4, \quad F = \frac{C_L}{C_{in}} = \frac{50 C_{ref}}{2 C_{ref}} = 25, \quad G = 1 \times \frac{5}{3} \times \frac{5}{3} \times 1 = \frac{25}{9}, \quad B = 2 \times 1 \times 1 \times 1 = 2, \quad s_1 = 2$$

$$H = GBF = \frac{5^4 \times 2}{9} \Rightarrow h = \sqrt[4]{H} = 5 \times \sqrt[4]{\frac{2}{9}} = 3.433$$

$$f_1 = 2.433, \quad f_2 = 2.060, \quad f_3 = 2.060, \quad f_4 = 3.433$$

$$s_2 = \left(\frac{f_1}{b_1}\right) \left(\frac{g_1}{g_2}\right) s_1 = 2.060, \quad s_3 = \left(\frac{f_2}{b_2}\right) \left(\frac{f_1}{b_1}\right) s_1 \left(\frac{g_1}{g_3}\right) = \frac{4.243}{\text{bR寸}} = \frac{24.278}{\text{cR寸}}$$

a. 输入电容 $2.060 C_{ref}$
 与 C_{in} 的比 1.030

b. 输入电容 $4.243 C_{ref}$
 与 C_{in} 的比 2.121

c. 输入电容 $24.278 C_{ref}$
 与 C_{in} 之比 12.139